

COMPOSITE VIDEO AMPLIFIERS

Easy solutions that bypass RF and IF circuitry
during vintage-TV Tests and Demonstrations.

For B&W Tube TV, a
Transistor Amplifier

Designed by Wayne Abare

For the CT-100, a
Tube Amplifier

Adapted by Pete Deksnis

Wayne Abare, presenter
Pete Deksnis, power point guy

In the Beginning...

When, in December 1953, the FCC approved folding color into the existing 1941 monochrome standard, broadcast stations scrambled to convert transmission systems to accommodate color.

To this end, manufacturers such as GE, Dumont, Dage, and RCA developed color monitors built around the first tricolor CRT available in reasonable quantity, the 15GP22.

Late in March 1954, RCA began the largest run of 15GP22-based color television sets ever produced. It was the Model CT-100, also known as the Merrill.

...in the beginning.

Few Merrills were sold to the public. Many languished in warehouses, others were assigned to RCA executives, stations, and NBC facilities. Jack Webb had one. Jack Benny reportedly had a blond Merrill. KING-TV in Seattle kept one in its transmitter building.

Only one is documented to have been sold to a consumer, although there were certainly others.

Mutt Color-Monitor

With so many Merrills unsold and with many placed in the hands of both RCA executives and NBC television network stations, it was only natural that the CT-100, designed for consumers, would be pressed into service as an over-the-air monitor for color broadcasters.

Why use a CT-100 to monitor composite video?

- Not only was the CT-100 readily available, it represented the culmination of a synergistic meld of business, science, engineering, manufacturing, and media. It was a magnificent example of state-of-the-art consumer electronics in 1954.
- No, it was not perfect. High voltage regulation was better in the 15-in. color Westinghouse H840CK15. Color sets took constant adjustment, although this was due in part to the broadcasters, who also were also in a learn-while-doing mode.
- However, color processing circuitry was second to none in the CT-100. True wideband color decoding gave, at least in theory, a sharper color rendition than the H840CK15's equal-band decoding. And, while a CBS 15-in. color set used the same wideband decoding as the CT-100, too few were made to satisfy the market for color monitors.

Mutt Color-Monitor

There would also be a need for an in-studio monitor that accepted composite video rather than a broadcast signal.

To that end, the CT-100 was often adapted to display composite video by modifying the CTC2 chassis used in a CT-100.

Rx-to-Monitor Schemes

Many methods were employed to inject a CT-100 chassis with composite video. The most simple was to connect the video signal directly to the control grid of the first video amplifier, a 6CL6.

This however is not recommended. The output of a CTC2 second detector is typically 6 Vp-p while the output of the RCA TX-1C colorplexer is specified as 1 Vp-p.

Clearly, an amplifier is required.


Rx-to-Monitor Schemes

It started early: of the two-hundred famous 1954 Rose Bowl sets, at least one -- RCA Model 5, serial number B570 -- was modified to accept composite video.

This set was updated by adding a 6J6 to the rear of the chassis. Little is known of the actual circuit, as the executive who used this set at the end of its useful NBC life had the 6J6 circuit stripped from the chassis.

Little more than a tube socket and the '6J6' chassis reference are left.


Rx-to-Monitor Schemes

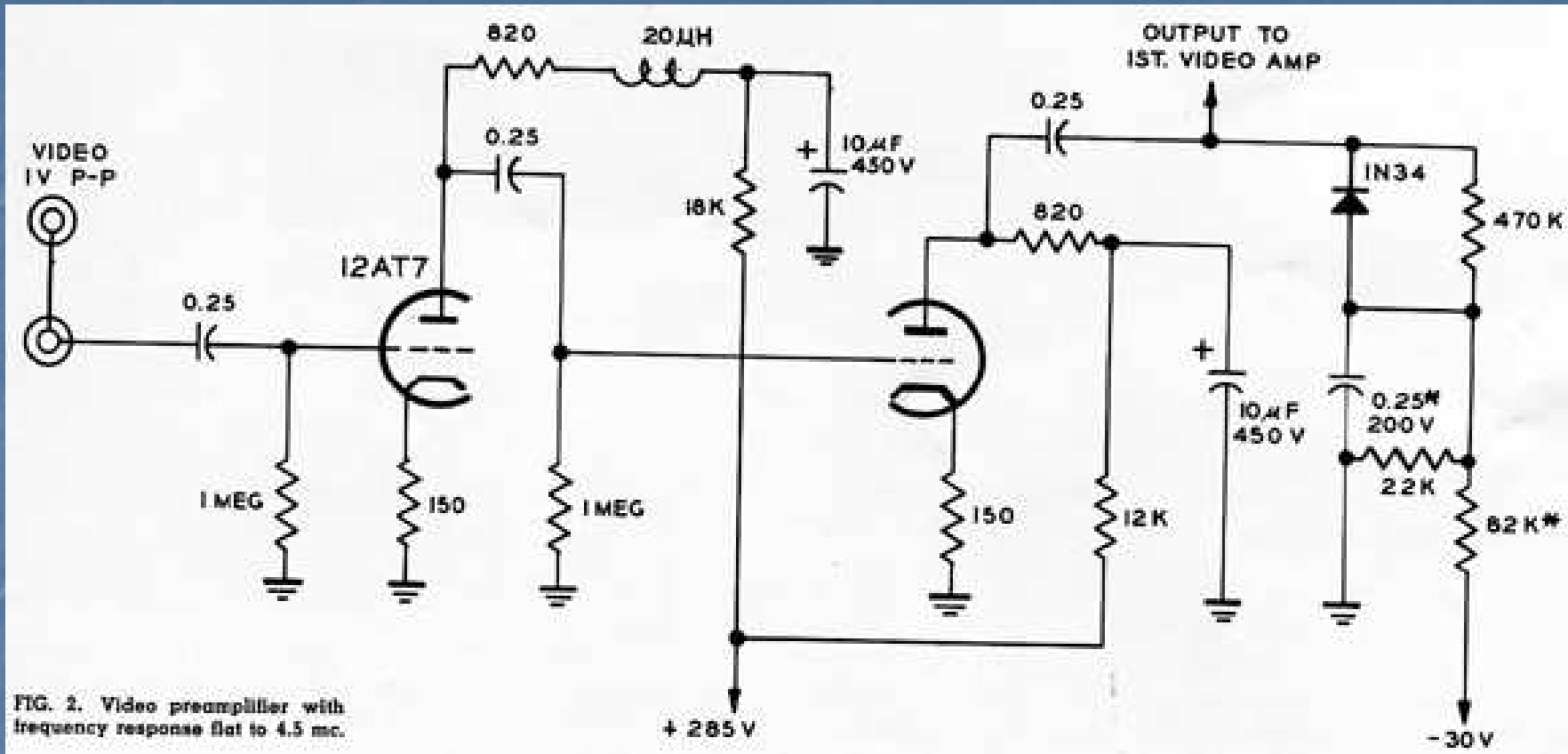

This is the original RCA Service Company circuit. Note in the lower right a minus 30-volt bias requirement for the amplifier. It is supplied by the CT-100.


In a 21-CT-55, a resistor and capacitor change value since, in that set, the negative bias voltage is 12 rather than 30.

Rx-to-Monitor Detail

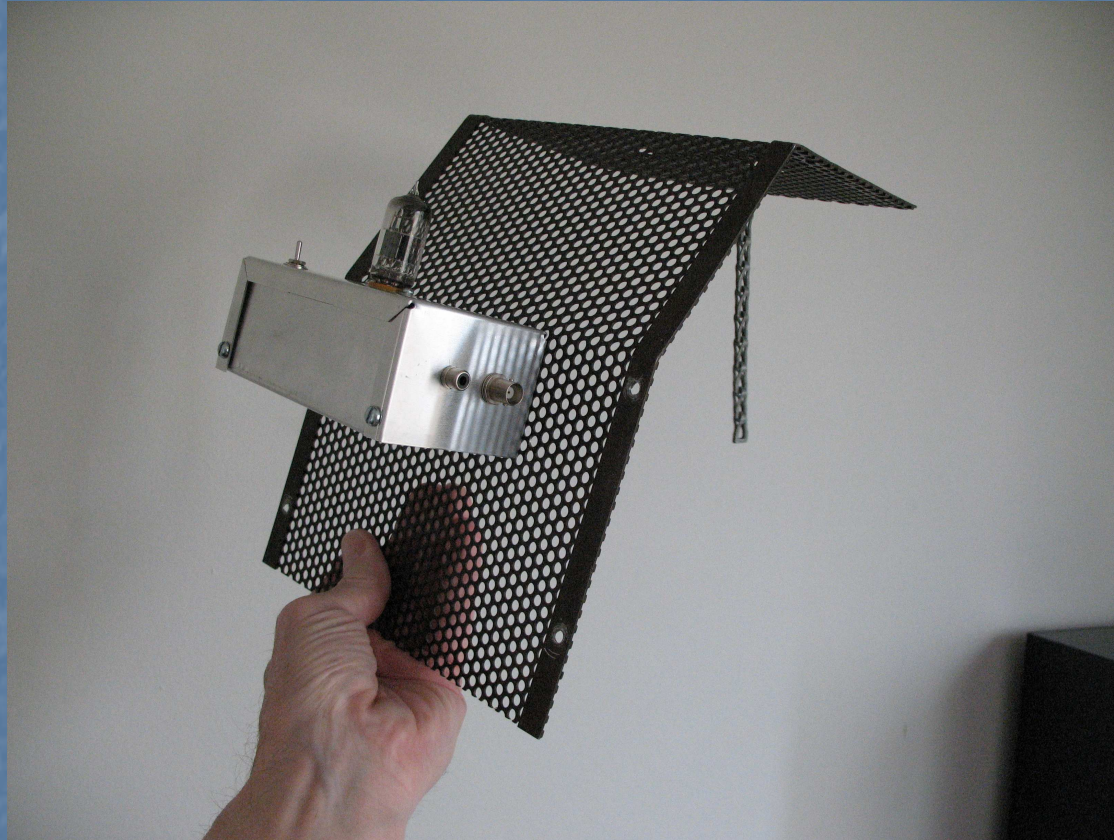


The composite video amplifier is built in a minibox and attached to the H-V cage. This is the first unit built and has provision for RCA and BNC input connectors.

Rx-to-Monitor Detail

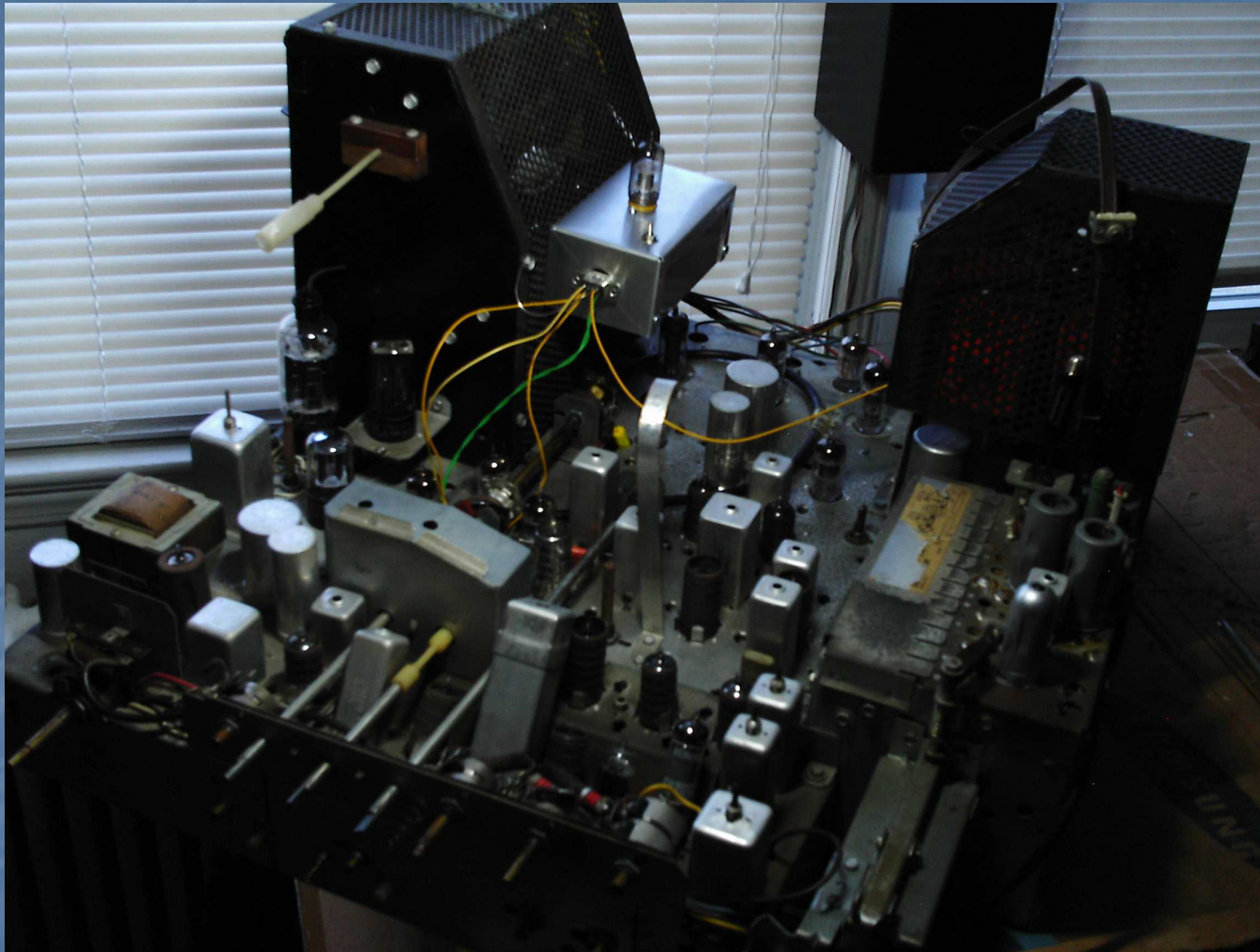


Filament power, ground, B+, negative bias, and relay control lines are needed for this installation. Radiation from the cage has not affected amplifier performance.

Rx-to-Monitor Detail

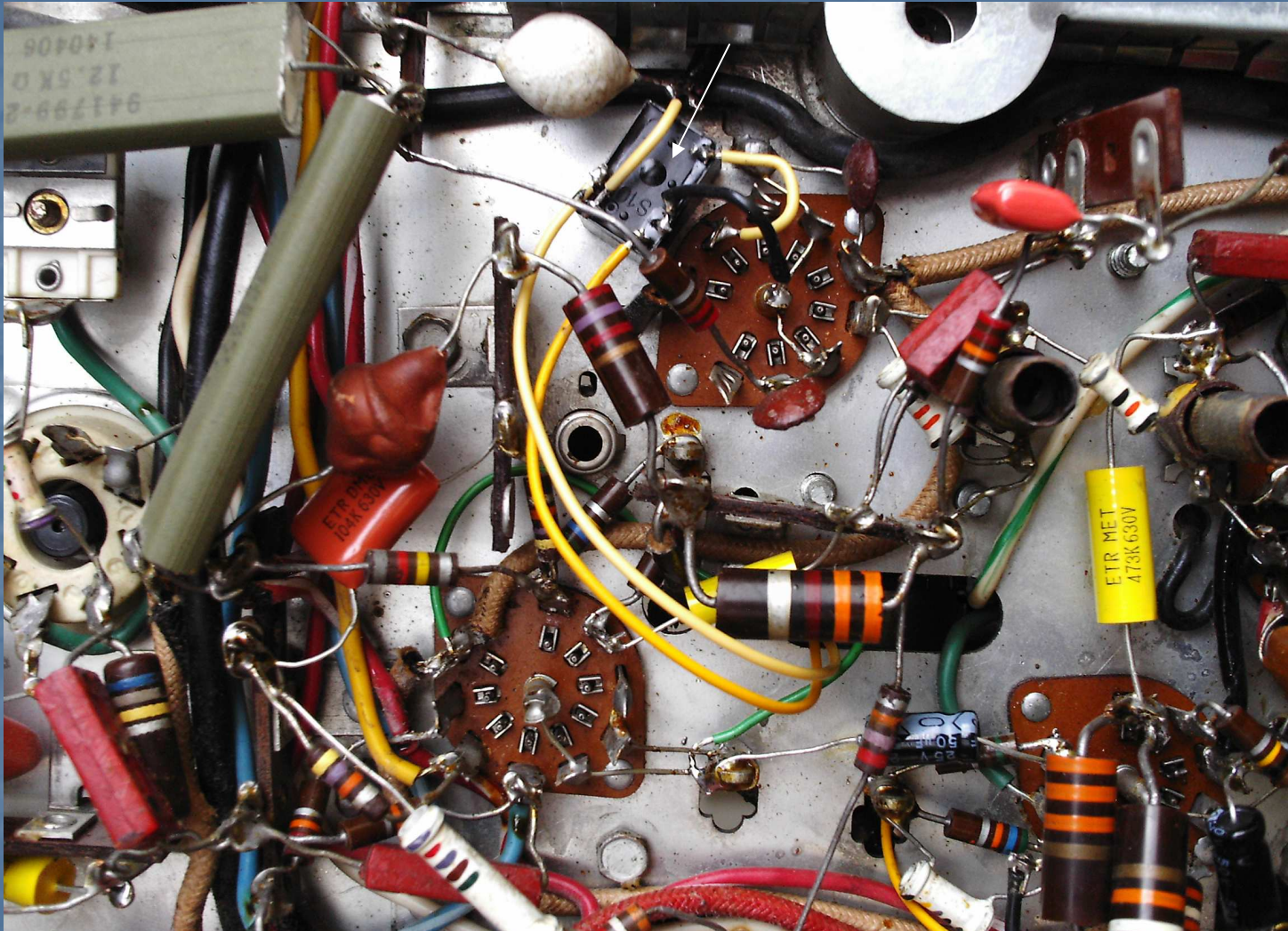

A small relay at the top center of the picture selects either the second detector or the composite video amplifier as a signal source for the first video amplifier in this CTC2 chassis.

Another look at the schematic...

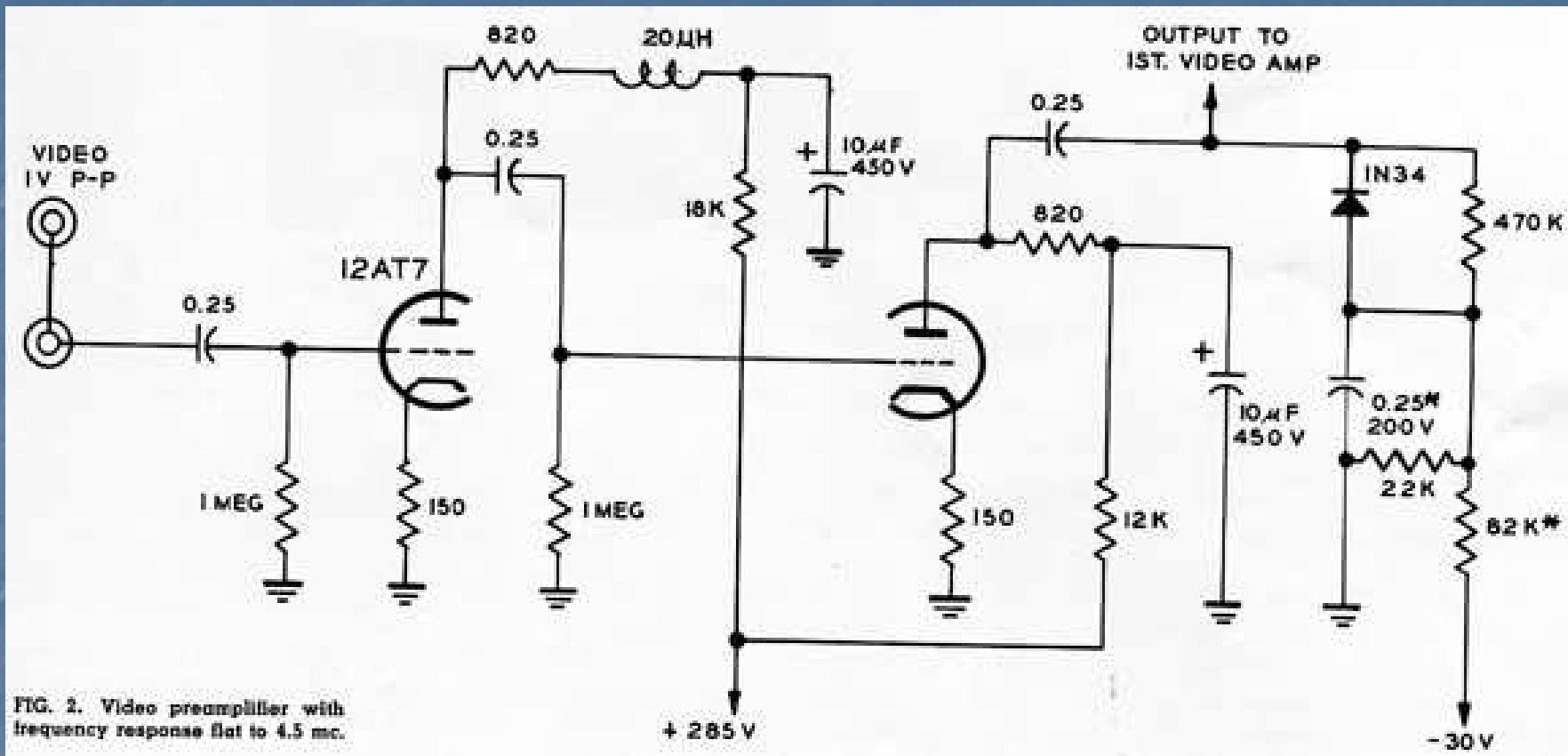

A caption in the lower left speaks of a flat response out to 4.5 MHz. It is achieved with a single shunt peaking coil in the first stage and the tiny plate load resistors -- only 820 ohms. With a healthy 12AT7, each stage has a gain of about three for a total of six volts out for one volt in. Because of the relatively low gain in each stage, the wide bandwidth is possible.

What's Next...?

For two years the composite interface adapter operated successfully in my CT-100. I had simplified the installation somewhat by using the under-chassis relay, which was driven by a small toggle switch on the minibox.


Why not somehow make the composite interface adapter portable. One that could be just plugged in without solder, drills, chassis punches, or any hard wiring.

Here's the Main Ingredient...



I found a bunch of 9-pin socket savers on eBay.

The Main Ingredient.

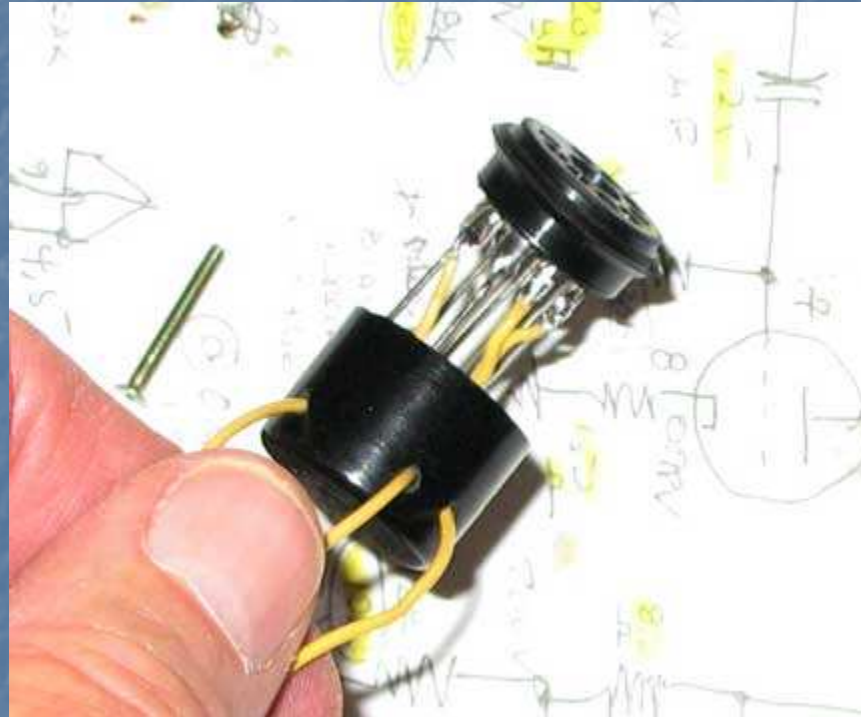

...and modified them to drive the composite interface adapter directly from the first video amplifier in the CTC2 chassis.

A Plug-n-Play CIA.



Pop out the 6CL6 first video amplifier and plug it into the socket saver.

A Plug-n-Play CIA.



Only the B+ is obtained from another location. An insulated alligator clip connects the adapter to +275 volts at the above-chassis contrast pot.

A Birdseye View...




Another operational CTC2 chassis testing the plug-n-play adapter.

Testing...


Two test were made on this new plug-n-play adapter.

A 5 MHz sweep.

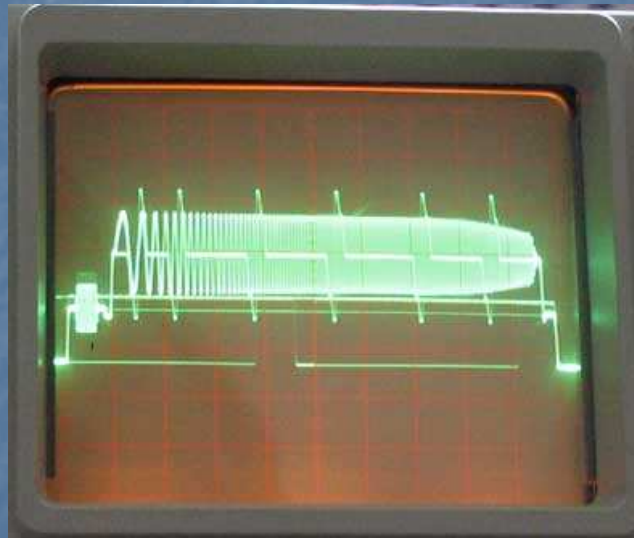

Testing...

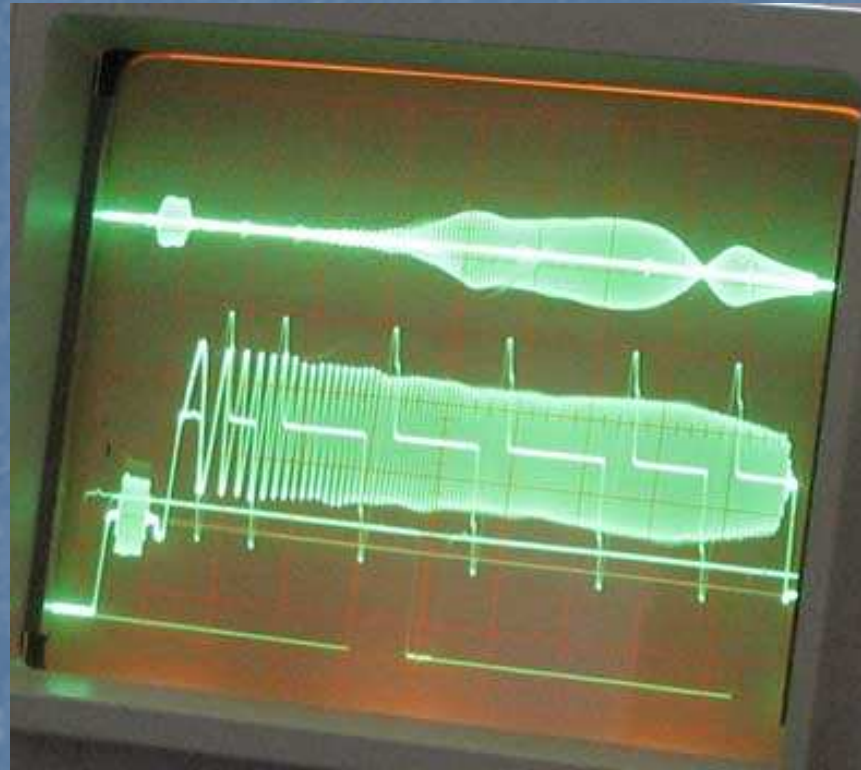The top trace is the output of the chroma amplifier receiving the full 5 MHz sweep. The notch is at 4.5 MHz to reduce interference from the sound carrier.



The 5 MHz sweep looked reasonable.

Testing...

However the effect of a 30-Hz square wave on the output was disappointing.



The top trace is the output of the first stage. The bottom trace is the output of the second stage, which is worse because it's a case of garbage-in, more garbage-out.

Improving the Low Frequency Response

I grabbed my copy of Grob *Basic Television* which is the text used in my first television course in tech school. Just what was needed.

Basically, the large phase angle that wants to form at the very lowest frequencies must be compensated for in a design balance that includes making the time constant of the plate decoupling RC network ten times better than the lowest video frequency, which is 30 cps in typical NTSC video amplifiers of the 40's and 50's.

Improving the Low Frequency Response


Additionally, the RC coupling network components can not simply be increased in value to meet low frequency requirements because tube physics issues become significant spoilers.

Improving the Low Frequency Response



The decoupling network for the first stage was modified by doubling the capacitance from 10- to 20- μ F. Notice how the top trace is becoming more square while the lower Trace improves too, a result of being driven by the improved waveform.

Improving the Low Frequency Response

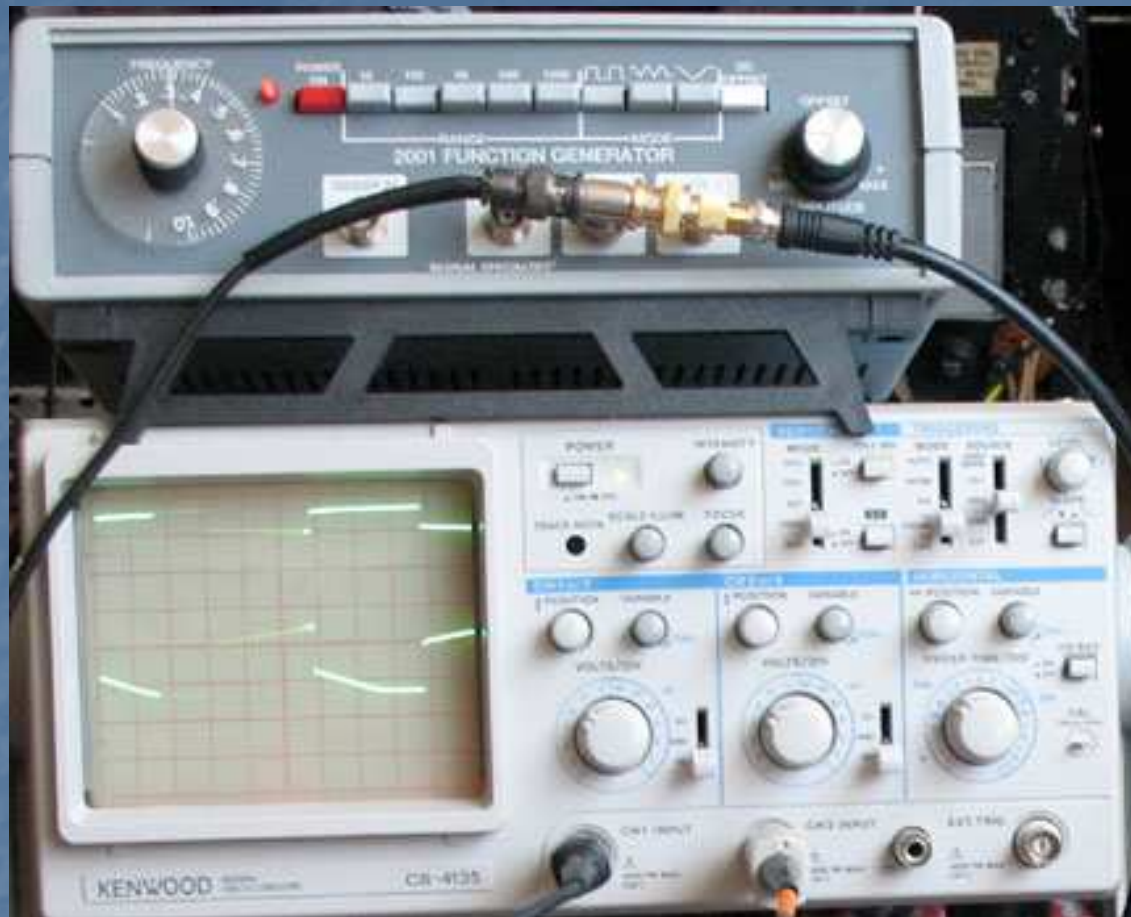


The decoupling network for the second stage was also modified by doubling the capacitance from 10- to 20- μ F. I also lowered the value of the grid resistors. The first stage (top) wave is now nearly eyeball-flat with concomitant second stage improvement. There are four changes that did the trick...

Improving the Low Frequency Response

The fix to the 1956 circuit:


- [1] first stage grid resistor decreased from 1 meg to 470K
- [2] second stage grid resistor decreased from 1 meg to 330K
- [3] first stage decoupling circuit capacitor increased from 10 to 20 μF
- [4] second stage decoupling circuit capacitor increased from 10 to 20 μF

One Final Refinement

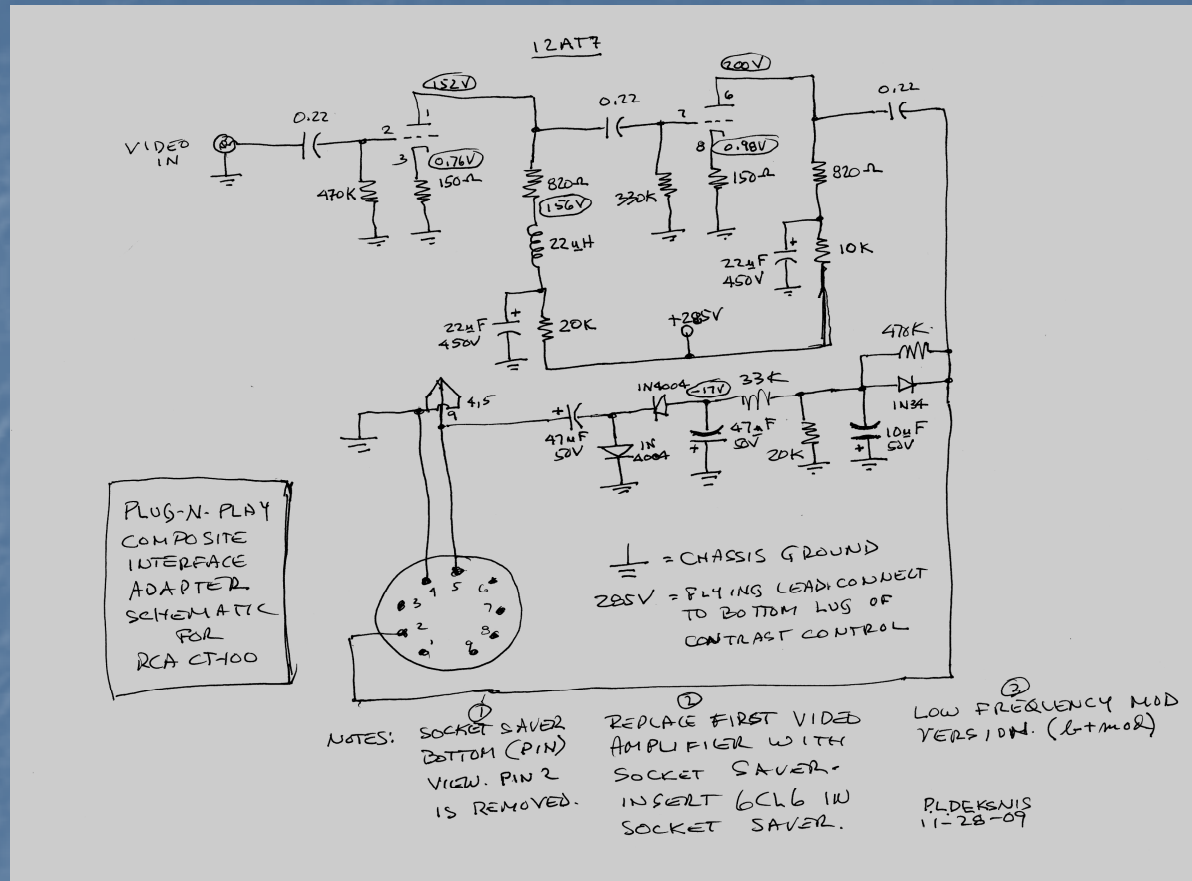

The circuit also includes a voltage doubler powered by the 6.3 Vac filament line. This eliminates the need to use the CTC2 as a negative bias source.

30 Hz Output
Input

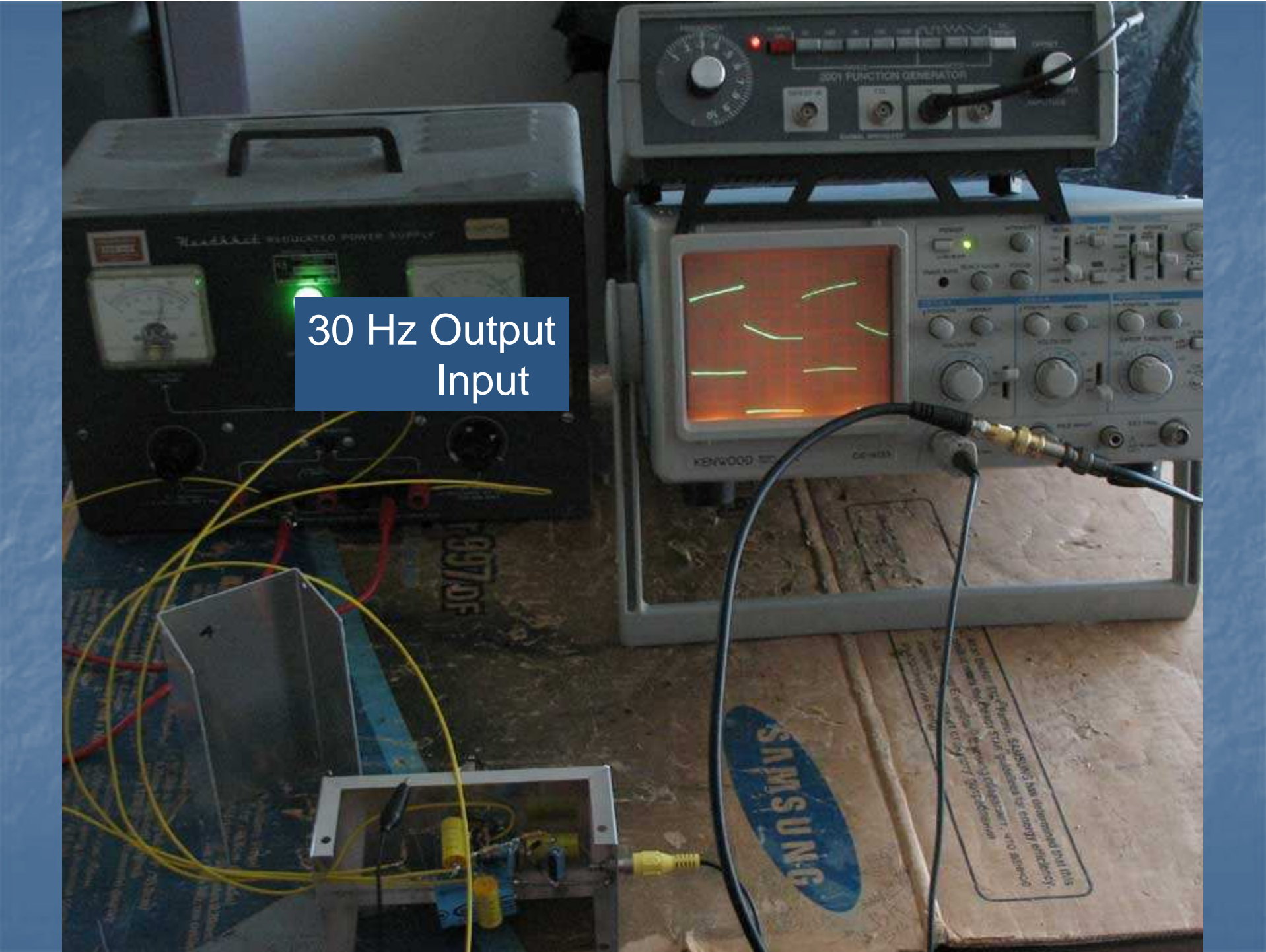

A total of nine Composite Interface Adapters were built.



The final run of six were produced in 2009.



Results...



