



*Servicing this popular attachment
can provide a new source of
revenue to servicemen.*

The Solovox keyboard installed on a standard upright piano.

By PAUL M. MILLER

THE *Solovox* piano attachment is becoming more popular with piano owners every day. Many thrilling tones are produced by this versatile electronic musical instrument. Although the owners of these fine instruments are seldom acquainted with such technical terms as "oscillator drift" and "negative pulse," they do recognize that the tone is "flat" or "off-key" and look to a radio repairman for service. *Solovox* owners hesitate to entrust their instrument to just any radio serviceman that happens to be handy. They would rather (and who can blame them) be assured that the man who gets their *Solovox* to repair or adjust is thoroughly familiar with its operation and maintenance.

There are two models of the *Solovox*—the old and the new—the Model J and the Model K. Basically they are similar.

The Model K has a few circuit changes that eliminate some of the oscillator adjustments, and has a new family of clarinet-like woodwind tones, controlled by a "Mute" key.

The modern Model K will be discussed here.

The *Solovox* is essentially an oscillator, and it all starts out with the 6SJ7 oscillator tube. This one tube controls all the notes on the keyboard. The oscillator operates at the highest octave of the audio frequencies that the instrument features, from 2093 to 3951 cycles per second.

Fig. 1, the wiring diagram, shows the keyboard and the oscillator circuit. The keys are attached to the tuning condensers grouped in series at the extreme left of the diagram.

Pressing any key inserts a certain amount of capacity into the oscillator grid circuit and tunes the oscillator to a particular frequency. Note that all similar musical letters on the keyboard in the three octaves are paralleled and note also that the low, middle, and high octave sections of the keyboard are each attached to a separate tuning contact bar. The reason for this is immediately apparent realizing that all keys of the three octaves of the same letters are in parallel and would produce the same note when

pushed down, if a tuning contact bar connected to a frequency divider were not present.

The note "C" (the first key) is the lowest frequency of the oscillator; the note "B" (the last key in the octave) is the highest frequency produced by the oscillator. The twelve condensers that tune the oscillator to the third or highest octave are all located in the "Vibrato box" attached to the keyboard. Examination of the diagram in Fig. 1 will reveal that in any octave on the keyboard there are twelve keys but only eleven contacts.

Key "B" in each octave has no contact.

When any one of the three "B" keys are depressed (or when no key is depressed) the oscillator is tuned to the highest frequency (3951 c.p.s.). The "C" keys tune the oscillator to its lowest frequency (2093 c.p.s.)

The oscillator tuning coil T_1 in Fig. 1, is the main tuning control of the *Solovox*. A powdered iron slug, moved in and out of the core of the coil, varying the inductance and therefore the frequency of the 6SJ7 oscillator. The only difference between this oscillator slug-tuned coil, and the oscillator coil in a receiver is that the slug has a long shaft and a knob at the end that extends to the outside of the cabinet so that the owner can "raise or lower the pitch" of the instrument. This is often necessary because few pianos are in perfect tune. Age of the piano, condition of piano and other factors will cause a noticeable difference between the piano and the *Solovox*—one of them will sound better.

(Continued on page 63)

Fig. 1. Wiring diagram of the Solovox showing the keyboard and the oscillator circuit. The keys are attached to tuning condensers shown at left of diagram.


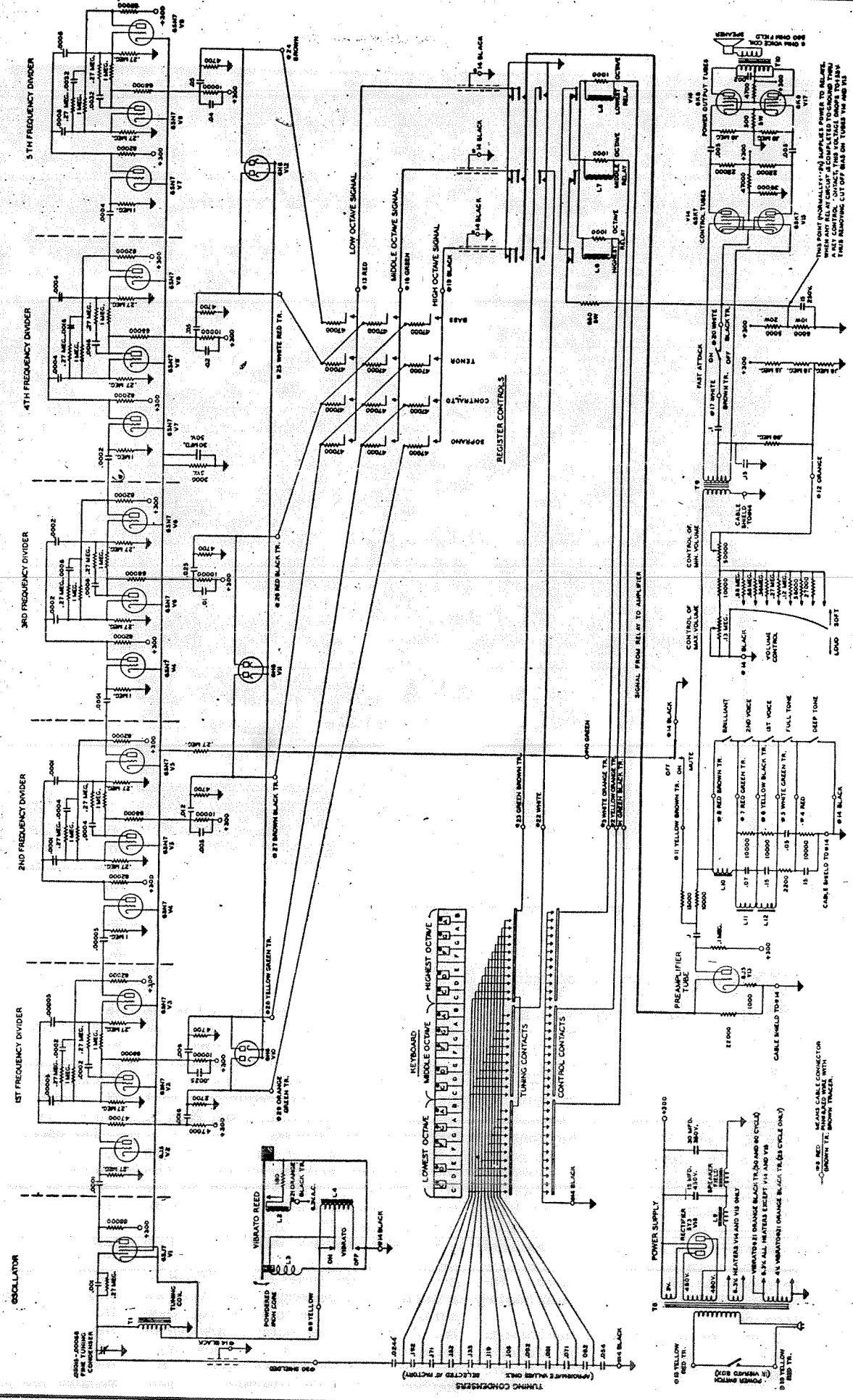


Fig. 2. Wiring diagram of the tone cabinet of the Solovox Model K.

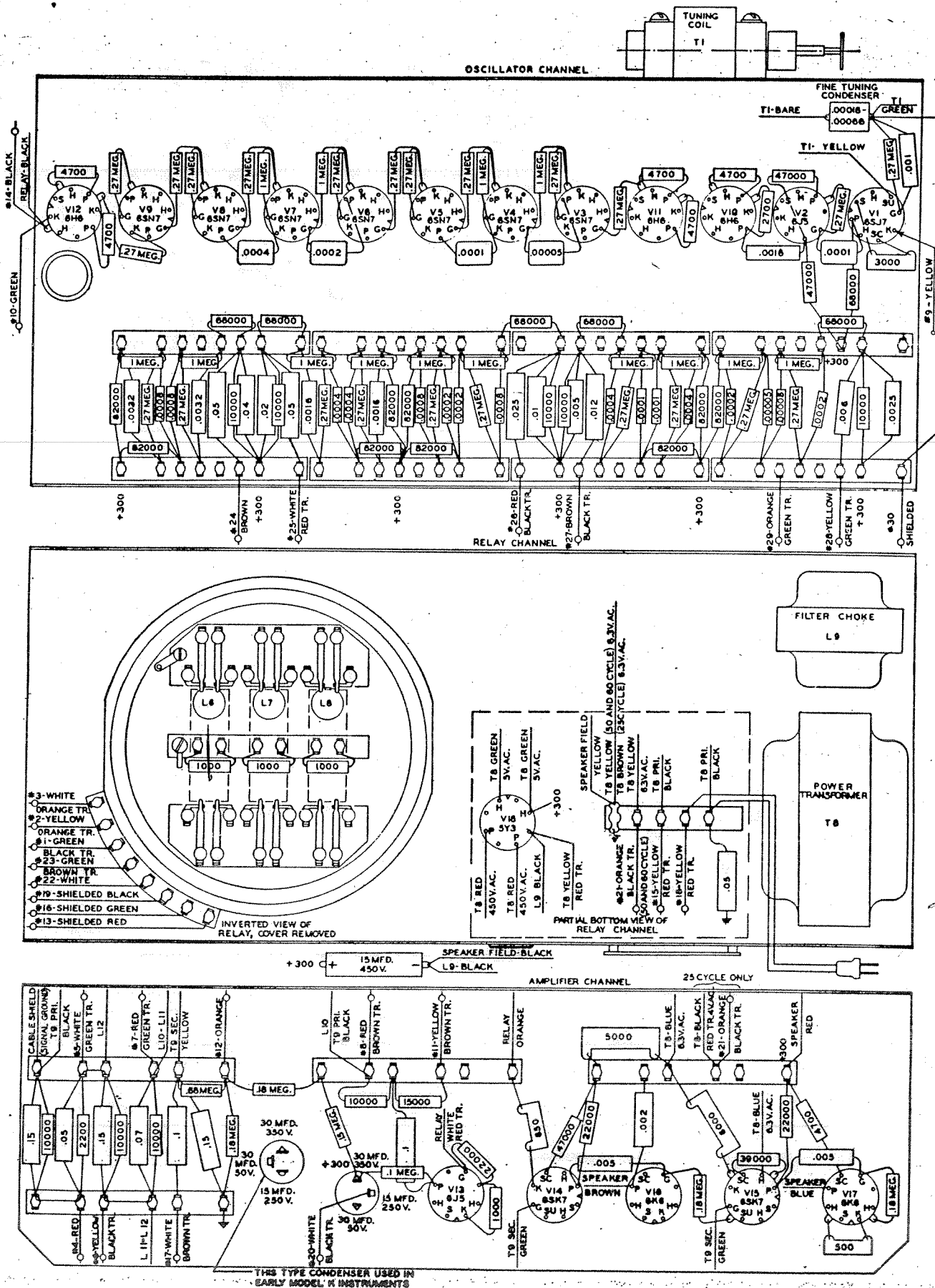

flat. This oscillator adjustment permits the user to tune both to a harmonious balance.

The "Vibrato" effect is one of the outstanding features that make the *Solovox* a musical instrument instead of merely a multi-toned oscillator. Any audio oscillator operating at a fixed frequency produces a pure solid note. In the *Solovox* the individual notes seem to quiver or vibrate, producing a musical note that is pleasing to the ear. The vibrato effect is incorporated in the *Solovox* by means of a coil with a movable iron core connected to a reed that is driven back and forth rapidly, like an automobile vibrator reed. This varies the inductance of the coil in regular and even amounts. This coil is connected to the tap on the master oscillator coil and thus varies the frequency of the oscillator.

The reed is started automatically, that is, when the volume control is pulled out to start the instrument operating, it starts the reed vibrating and the magnetic drive keeps it going. It is a silent mechanism. The vibrato reed and its associated circuit can be seen in Figs. 1 and 3.

The Frequency Dividers

The output (2093-3951 c.p.s.) of the master oscillator is fed to a series of frequency dividers connected in cascade fashion.




Close-up view of the Solovox keyboard as it is attached to the piano.

Each frequency divider divides its input frequency in half, producing a note one octave lower than its input note. Looking at Fig. 1 it is seen that each frequency divider stage is comprised of three triodes. In the first stage the 6J5 triode acts as a driver and pulse rectifier, supplying sharp

and narrow negative pulses to actuate a symmetrical feedback tripping circuit made up of two triodes in one envelope (6SN7). The driver of the balance of the stages is one half of a 6SN7.

Either section of the twin triode can
(Continued on page 136)

Fig. 3. Wiring diagram of the Solovox keyboard unit.

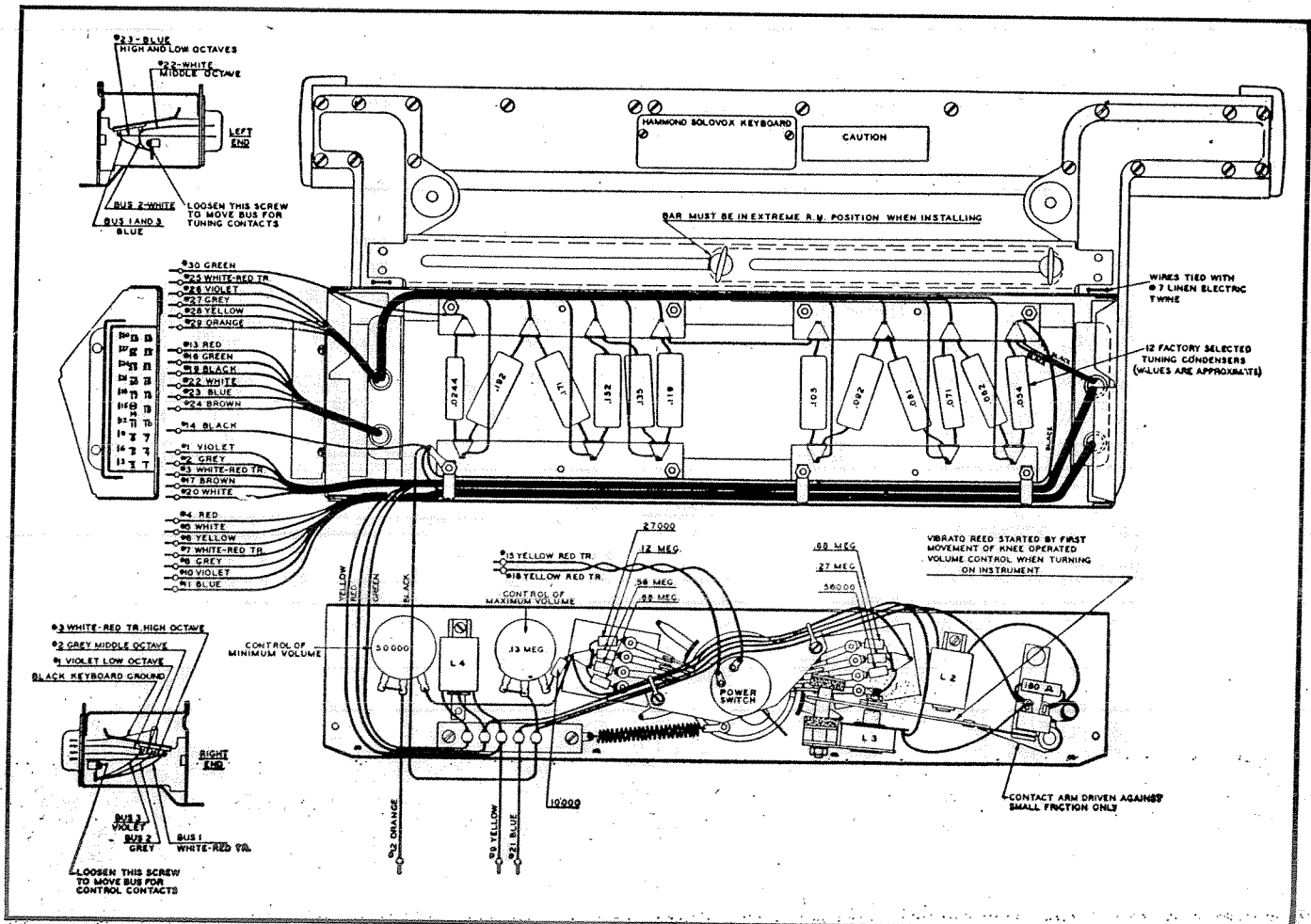


ANNOUNCING

A COMPLETE LINE OF
ASTATIC
Long-Playing PICKUPS
and CARTRIDGES
that includes JUST WHAT
YOU'RE LOOKING FOR!



FLT-33 CRYSTAL
TRANSCRIPTION
PICKUP

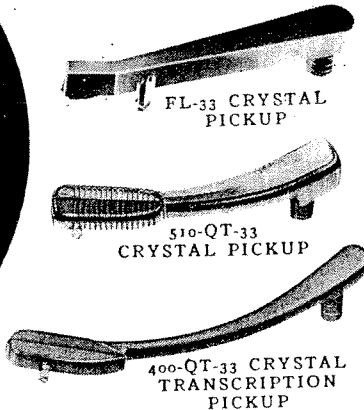

FL-33 CRYSTAL
PICKUP
510-QT-33
CRYSTAL PICKUP
400-QT-33 CRYSTAL
TRANSCRIPTION
PICKUP

WANT a two-in-one pickup that plays both LP and 78 RPM Records with the simple switching of cartridges . . . so simple that a child can make the change in a few seconds? Or, perhaps you are looking for comparable reproduction quality, with more emphasis on economy? Regardless of whether your requirements point to cartridges employing ceramic elements or magnetic-type units . . . whether you prefer permanent or replaceable needles, metal, sapphire or diamond . . . whether cost is first or secondary . . . whatever the conditions to be met—there now is a unit of Astatic precision engineering and construction, that will exactly fill the bill. Space permits mention here of only a few. Why not write for new brochure, giving complete information, illustrations, on the Astatic Long-Playing Equipment Line?

Astatic Crystal Devices
Manufactured Under Brush
Development Co. Patents

Listed in the Radio Industry Red Book




SENSATIONALLY DIFFERENT... SLIM JIM

A revolutionary development in soldering irons is the inter-changeable Thermo-Cel head. These heads not only simplify difficult operations but also are available in different wattages, thus giving the operator a flexibility of many irons in one. Our fifty-watt head will do the work of any ordinary 100-watt standard iron. **SAVE MONEY — SAVE TIME — LESSEN FATIGUE — INCREASE SPEED AND EFFICIENCY** — try the SLIM JIM and you'll never go back to old, heavy, hot-handled antiques. **THE SLIM JIM IS MADE TO STAND UP UNDER THE MOST EXACTING, CONTINUOUS 24-hour DUTY REQUIREMENTS.**

WEIGHT OF IRON
3 1/2 OZ.

JOBBER: WRITE
DEPT. R-11
FOR DETAILS

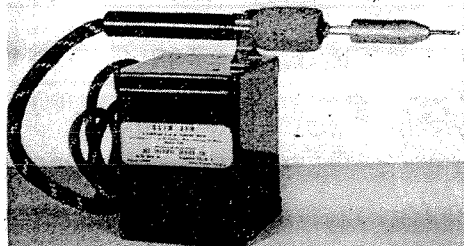

JOBBERS: Many choice areas open. Write for details. Unit as pictured above—complete—\$14.50 list. Less transformer—for 6-volt battery—\$9.95 list.

Note how specially developed sturdy Current Conductors are plugged into iron. Heat is thereby concentrated in Thermo-Cell. Air space minimizes back-flow of heat, thus assuring a cool handle at all times.

For General Soldering Jewelry Instruments

SLIM JIM Thermo-Cel heads are equipped with the new "Filmed" tip—a special process developed by us—to prevent scale from oxidation, from "freezing" the tip in the head. This added feature also increases the life of the tip from 5 to 10 times longer. The SLIM JIM has never "broken down," either in the "field" or under the rigid test conditions in our laboratory.

The SLIM JIM is ideal for use in emergency. The iron can be purchased without the transformer, and with battery clip, for use on any 6-volt battery. Write for details to Dept. BB.

98% OF THE HEAT IN THE TIP

CHOOSE YOUR THERMO-CEL for the JOB — Easily Changed

L-RAMJET—1/4" or 3/16"



FOR: RADIO ASSEMBLY — SWITCH BOARDS — REPAIRS — METERS

Z-BULLET—1/8"—3/16"



FOR: HIGH SPEED ASSEMBLY — VOICE COILS — PICKUPS — METERS — HEARING AIDS

U-HEAVY OBLIQUE—3/16"—1/4"



FOR: TERMINAL BOARDS — RELAYS — CONTACTS

A-LIGHT OBLIQUE—1/4"—3/16"



FOR: PRECISION SOLDERING — OFF ANGLE JOBS — INSTRUMENTS

JET THERMAL DEVICE CO.
2173 86th STREET BROOKLYN, N. Y.

The Solovox (Continued from page 63)

be conducting at any one particular moment. When one triode is conducting, it is drawing plate current and the resulting voltage drop across the plate load resistor biases the other triode to cut-off and holds it there until the driver sends another negative pulse to the grids of the twin triode. Since one triode is already in a cut-off condition, this negative pulse will have no effect on it, but it will drive the other triode to cut-off condition. When this triode suddenly stops conducting and therefore stops drawing plate current, a positive pulse is produced at the plate terminal of this triode.

This positive pulse appears at the grid of the second triode and it starts to conduct. The instant it starts to conduct and draw plate current, a negative pulse is produced at its plate and this negative pulse is fed back to the grid of the first tube to insure a cut-off condition until the next cycle.

The next input pulse from the driver will have no effect on the first triode (this time) but drives the second triode to cut-off and then starts the first triode conducting. From this it can be seen that two input cycles are necessary to produce one output cycle. This looks rather complicated as it is written in a lot of words, but following the action on the diagram makes it very simple.

The output of the second triode in any divider stage is fed to the grid of the driver of the next stage. Note that the coupling condenser values are doubled in the progressive stages as the frequency is halved.

Now we press a key on the keyboard, a "C" key for instance. Any one of the "C" keys we push down will tune the oscillator to the same frequency by inserting the .0244 μ f. condenser in the strip of twelve, and tuning the oscillator. The oscillator is oscillating and activating all of the frequency divider stages. Let us assume that the audio system is silent for a moment—waiting for the system to select one note out of many that are ready to be admitted, while we follow the path of the note that we chose.

Underneath the keyboard tuning contacts on the diagram are the "Control Contacts." If we depressed the "C" key in the lowest octave, the No. 3 or lowest octave relay is actuated, and all of the frequency dividers are tuned to "C" by the capacitance that is thrown into the grid circuit of the 6SJ7 oscillator tube.

Off the plate of the second frequency divider comes the signal and down to the low octave section of the "Register Controls" through a 47,000 ohm resistor and through the relay to the grid of the preamplifier tube, and on into the control tubes to the audio output 6K6's. At the same moment we pressed the key the low octave relay went

into operation and removed the cut-off bias from the control tubes—permitting the signal to enter. This action is described in detail later in the article.

Sound Effects

That note we just released through the *Solovox* was a single note (for purposes of explanation). Now how do we get those beautiful organ tones and other sound effects that create depth and fine tone qualities? When we depressed the key to send our "C" note on its way through the circuit, we also tuned all of the frequency dividers, as noted before, to "C"—but in different octaves. The output of the rest of these dividers is not used at present but if we want the above effects all we have to do is to add the output of one or more of these dividers to the preamplifier input by pressing the "Contralto," "Tenor," "Bass" buttons, and the signals (an octave apart) come through the 47,000 ohm resistor, mix with the original signal, and the composite signal goes on into the preamplifier input grid.

Naturally if two keys are pressed on the keyboard in any octave, some undesirable notes would be created if it were not for a section of the relay that prevents this by selecting only the lower pitched note in such cases.

Between the preamplifier tube and the volume control on the diagram is a switch labeled "Mute." It is shown in the normal position in the diagram, grounding the 6H6 cathodes. Throwing the switch on disconnects the diodes. The odd harmonics of the frequency dividers, which sound like a clarinet, are then produced.

Following the preamplifier is a group of condensers, resistors, and chokes and the controls labeled "Deep Tone," etc., that insert various combinations of resistance, capacity, and inductance into the line to change the characteristics of the signal going to the power amplifiers. For instance; the "Full Tone" contact attenuates some of the high frequencies but does not affect the low or medium frequencies. Other combinations affect the "curve" of the note in other sections. Similar to the tone and treble controls in a radio or public address system, the effects are very pleasing to the ear.

Remembering the "vibrato," magnetically driven reed, we can readily appreciate the range and tone of the *Solovox*. This vibrato reed might be compared to an FM sweep generator, but mechanical in operation and in the audio frequency range.

Control Tubes

Almost any amplifier will pick up and amplify hum, microphonics, and other noises of an undesirable nature, but in the *Solovox*, a unique circuit arrangement prevents any such disturbances from sounding through the speaker—when no key is pressed the *Solovox* is perfectly silent. The normal cathode voltage on the 6SK7 control tubes is .175 volts positive cut-off.

BEST BUYS—KITS—PARTS—ACCESSORIES—LOWEST PRICES




POWER SUPPLY FOR ANY 274-N RECEIVER

Here it is—at last! Just plug it into the rear of your 274-N RECEIVER... any model! Complete kit, and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. All conversion parts included. (Resistance-filter Kit \$6.95) Standard model has choke filter..... \$7.95

BC-454—3—6 MC.

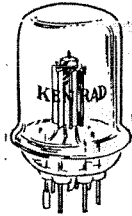Brand new sealed cartons with tubes, diagram and instructions included, for converting to 10 Mceters. ONLY..... \$5.95 ea.



VHF SURPLUS TUBES

FILAMENTS TESTED BEFORE SHIPMENT! ALL BRAND NEW!

826 UHF Triode. Full ratings (86 watts output) up to 250 mcl 1000 v. plate @ 125 ma. Get real power on 2 meters with a pair of these tubes. All tubes BRAND NEW! Get yours NOW at only 75c ea. or 4 for \$2.40.

RCA 8012 VHF Triode. TANTALUM plate and Tantalum grid 35 watts output. 40 watts Plate Dissipation. Used as osc. or amp. at full ratings (1000v. @ 80ma.) up to 500 MEG! Double plate and grid connections allow balanced circuit design. High "Q" lines and simplifies neutralization. C.T. 6.3v. Filament reduces filament lead inductance. All Brand NEW! Reg. price \$14.50. Surplus price while they last, only \$2.45 ea. or 4 for \$8.40.

WE316A VHF Triode. Brand NEW! Commonly called the "door-knob" this triode is outstanding for VHF. 30 watts plate dissipation. Used as oscillator to 1000 MEG. 450 plate @ 80 ma. 7 1/2 watts output at 500 MEG! Reg. price \$18.50. Our very low price 79c ea. or 4 for \$3.00.

WE717A PENTODE. Hams know this tube's ability to "soup up" any receiver. Has transconductance of 4,000 and is directly interchangeable with 6SK7. Low loss base and ultra-short leads allow this tube to function better at high frequencies. ALL BRAND NEW! Orig. cost \$3.75 ea. Your price 98c ea. or 4 for \$3.25.

829B TWIN BEAM TETRODE. This well known tube is ideal for application at VHF. Full output (87 watts) up to 200 MEG! 750v. plate @ 240ma. 6.3v. or 12.6v. filament. BRAND NEW! Your Cost \$3.95 ea. or 4 for \$13.50.

CERAMIC SOCKET for 829B, 832 etc. 49c ea.

832A TWIN BEAM TETRODE. (Not pictured) 26 watts output up to 200 MEG! 750v. @ 90 ma. 6.3 or 12.6v. fil. BRAND NEW! \$2.50 ea. or 4 for \$8.40.

OTHER TUBES NOT PICTURED

807 Beam Tetrode. This popular tube hardly requires any explanation. One of the most popular tubes for r.f. application. Brand new. \$1.12 ea. or 4 for \$3.95.

810 Power Triode. This tube is a real powerhouse! 575 watts output up to 30 mcl! Carbon anode. Grid out of side of envelope for max. h.f. efficiency. BRAND NEW! Only \$5.95 ea. or 4 for \$21.95.

815 Twin Beam Tetrode. Full ratings (56 watts output) up to 125 mcl! Requires only .18 watt grid driving power for full output. A very versatile tube for most any h.f. application. Brand new. Only \$2.50 ea. or 4 for \$9.20.

NAVY SPARE-PARTS CHEST WITH MANY FINE PARTS

• At least \$25.00 worth of BRAND NEW, excellent parts, and a plywood chest, gray lacquered, with lift compartment, handles and hasp, at a give-away price. \$4.95 net! Chest contains audio xifiers, caps, mica condensers, oil condensers, coils, relay parts, wire-wound rheostats, 3 Type 78 Tubes, 2 Type 77 and 1 RCA-1642. EVERYTHING BRAND NEW! VERY FEW ON HAND. Air-Mail your order..... \$4.95




SIGMA HERMETICALLY SEALED 7000 OHM SPDT RELAYS!



Operates on 1 ma. current change. This relay requires no maintenance as all moving parts and contacts are in a VACUUM! Manufactured by SIGMA, this relay spells TOPS in performance. Contact ratings, 1 amp. Used in photoelectric equipment, remote control, receivers, etc. Heavy wire lead connections. Spade bolt mtg. simplifies installation. Govt. cost many times our low price of only \$1.95 ea. 10 for \$17.00.

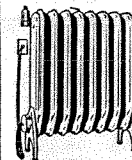
SIGMA PLUG-IN RELAY (not pictured) 2,000 ohm coil. Contacts SPDT 1 amp. Plugs into standard 5 prong tube socket. Enclosed in aluminum can 1 1/2" x 1 1/2" x 2 1/2". Excellent multi-purpose relay. A BUY AT \$1.50 ea. or 5 for \$6.25.



ELECTRETEEM HEATERS. 60% DISCOUNT! FORMER PRICE \$37.35 NOW ONLY \$14.94 ea. ONLY A FEW ON HAND! ORDER NOW!

Brand New 110v. 900 watt Portable Electric STEAM heaters made by Electreteam Radiator Corp. Measures 20" x 23" x 7 1/4". Nickel-chrome element. Steel shell, bonderized against rust. Wt. 39 lbs. Easy to carry. Under boiler holds 2 qts. water. Just plug it in. Underwriters Lab. approved. Operates on AC or DC. Oven Baked Enamel Finish. No moving parts to get out of order. Gives man-size heat at low power consumption. ONLY \$14.94 ea.

SMALL PRECISION LATHE—110-V. A.C.

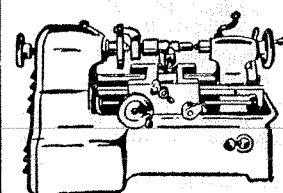

FORMERLY SOLD FOR \$60.75
NEW LOW PRICE NOW \$41.50

A small lathe for radio shops, jewelers, laboratories, hobby-writers, Lab. approved. Operates on AC or DC. Automatic Feed. Work capacity 3" between centers. Swing over bed 2". Constructed of steel and cast iron. Accurately machined and finished. Fan-Cooled Motor mounted inside the base. Complete with 1 1/2" face plate, 2 lathe centers, tool post and rockler, one lathe dog, one tool-bit and test rod.

COMPLETE ACCESSORY KIT

Including 4-jaw chuck, drill chuck, countersink drill, 2 tool-bits, 2 lathe dogs, 1 face plate with 8 drilled and tapped holes, 4 collets, 1 collet chuck, 1 Allen wrench. FORMER PRICE \$36.25. NEW LOW PRICE ONLY \$24.50.



IMPEDANCE MATCHING TRANSFORMER


Changes any low impedance headset to high impedance. Very compact, has standard plug attached for insertion into a standard headphone jack in receiver. Jack on front of impedance matching box, accepts standard headset plug. Make use of your low impedance headsets. Get yours while quantity lasts. ALL BRAND NEW! 2 for \$1.15 POSTPAID.

HANDSET HANGERS
in black crackle finish
\$1.95 ea.




REST-A-PHONE

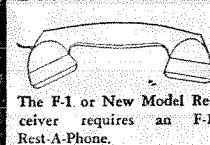Snaps on your receiver in 5 seconds!
Balances on the shoulder



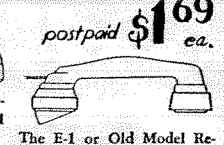The F-1 or New Model Receiver requires an F-1 Rest-A-Phone.



The E-1 or Old Model Receiver requires an E-1 Rest-A-Phone.

postpaid \$1.69 ea.

★ 4-HOUR MAIL-ORDER SERVICE. WE SHIP ANYWHERE.
20% DEPOSIT MUST ACCOMPANY ALL ORDERS, BALANCE C.O.D.

OFFENBACH & REIMUS CO.

372 ELLIS ST. SAN FRANCISCO, CALIF.

'PHONE—Ordway 3-8551

LOOK at these BIG VALUES!

3-Post Intermix Record Changer

Made by Seeburg for a prominent manufacturer. Has all the BIG features. 10" and 12" records may be intermixed. Automatic stop turns off changer after last record. Control switch for reject, automatic and manual, "off" and "start". This is one of the finest changers ever made. Pickup arm complete with Astatic QTM cartridge. Perfect for either replacement or for building your own high-quality record player. . . . Only **\$2650**



MAGNETIC PICKUP ARM

Hi-impedance magnetic phono pickup arm. Has variable adjustment for low record wear. Provides highest quality output. Priced far less than cost of many inferior units. . . . **\$139**

455 KC I. F. Transformers

A real buy in standard replacement units. 8" x 1 1/2" square. Stock up now! **38c** each. **\$100** for 3 for only

SAVE MONEY on PARTS KITS

- (1) 100 asstd. mica condensers; pigtail and lug types. .00005 to .01 mfd . . . **\$1.95**
 - (2) 40 asstd. push-on knobs for knurled shafts. Red, green, walnut, ivory . . . **\$1.29**
 - (3) 25 asstd. 10 and 20 watt vitreous enameled resistors. Values up to 25,000 ohms. No two alike **\$1.69**
 - (4) 100 asstd. 1/2-1-2 watt carbon resistors. All RMA color-coded. Most popular values **\$1.49**
- ORDER BY KIT NUMBER!**

Value of the Year!

100 MICROAMPERE METERS

Made by Simpson especially for use in famous I-166 Test Set. 100 microamp full-scale deflection; 1000-ohm internal resistance. 3" round bakelite case. Scale is calibrated for ohms, DC volts and AC volts. Complete with diagram for volts-ohm-milliammeter. Brand new and worth several times this low price **\$550**


REPLACEMENT FILTER CONDENSERS

20-20 mfd 150 WVDC (4 leads) **48¢** each—10 for **\$4.50**
8- 8 mfd 450 WVDC (3 leads) **48¢** each—10 for **\$4.50**

LINE CORD SPECIAL

6 ft. brown rubber cord with brown bakelite plug. Finest quality at lowest cost. Have 'em on hand. **13¢** each. 10 for **\$100**

SPEAKER VALUES

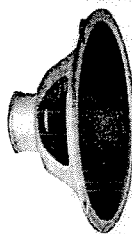

5" PM, heavy duty type; 1.47 oz. Alnico 5 magnet; 3/4" voice coil. Rated 5 watts. **ONLY \$140**
4" x 6" PM, Alnico 5, 1 oz. mag-net. Fine replacement speaker **\$140**

PUBLIC ADDRESS SPEAKERS

10" PM, 18 oz. Alnico 3 magnet. Rated 10-12 watts . . . **\$445**
12" PM, 6.8 oz. Alnico 8 magnet. Rated 14-18 watts . . . **\$595**
12" dynamic speaker with 900-ohm field. Rated 15 watts. Excellent tonal response. A bargain **\$695**

ORDER FROM THIS AD!

Select what you need from the big values listed here—and send your order now! Quantities are limited. Send 25% deposit with order. We ship C. O. D. for balance, all advertised items F.O.B. Chicago. GET YOUR NAME IN OUR MAILING LIST. We carry complete stock PA equipment—BOGAN, MASCO Amplifiers—Shure, Turner Mikes—University Speakers, etc. Write for complete list.

NATION WIDE RADIO
(The Serviceman's Supply House)
572 W. Randolph Street
CHICAGO 6, ILLINOIS

This bias voltage is obtained from the resistors forming the voltage divider attached to the cathodes, the 5000 and 6000 ohm resistors.

When a key is pressed, the relay shunts the 6000 ohm resistor with the resistance of the relay coil, reducing the bias voltage to about 55 volts and the control tubes are no longer cut off, and the "gate is open" for the note to pass through.

The 15 µfd. condenser in parallel with the divider prevents surges, plops, and clicks and makes the entry and departure of the note into the control grids smooth. Fast attack and slow attack is obtained by throwing the .1 µfd. condenser in series with the cathode in or out of the circuit.

Although the depressing of any key throws this cut-off bias off the control tubes, it determines only the matter of signal or no signal, and not how much signal. This is taken care of by the volume control which is also part of the voltage divider furnishing bias to the control tubes. This group of resistors in parallel determines how much operating bias and therefore regulates the gain. It is not an ordi-

nary volume control and not subject to the vagaries of such.

A variable control of minimum volume and maximum volume is incorporated in series with this master volume control and is set for the customer's preference. They will vary according to the customer and the location of the instrument. These adjustments may require setting (resetting) if the *Solovox* is moved, for instance, from the living room of a private home to a large auditorium with quite different acoustics.

Full understanding of "How It Works" will enable most servicemen to satisfy many of the customer complaints that will arise—by making a few simple adjustments that the customer does not know about, or has forgotten. Often the instruction book gets lost or mislaid and the owner brings the instrument in for service rather than trust to memory.

Any serviceman who plans on going out after *Solovox* business, and there is plenty of it, should have all the dope before attempting any repairs or adjustments.

-30-

Radio Service

(Continued from page 57)

Television service will tie-in perfectly with your regular work, provided you have the equipment and knowledge necessary. Charges for this type of service will be high, in accordance with the high cost of the sets. Installation of television antenna arrays is a business by itself!

Test instruments are all expensive. Some of them are out of sight for most of us—but—please select the best you can. Stay away from these bargain testers, the pretty but cheaply made


ones. A good instrument, though costly, will be accurate and last longer, and will add to your prestige as a radioman.

The following is a list of instruments for the up-to-date service shop. They are suggested as a means of fast, accurate and profitable work. The well equipped shop should have; a test speaker, a v.t.v.m., a signal generator, oscillograph, tube tester, and a sweep signal generator (for television).

In addition to these instruments, the shop should have a portable tube checker and multimeter. These can be of the cheaper variety as they are used for outside work and are subjected to much abuse.

-30-

Fig. 5. Another view of the test bench. By panel-mounting all test instruments the workbench surface is kept clear and the servicing work is expedited.

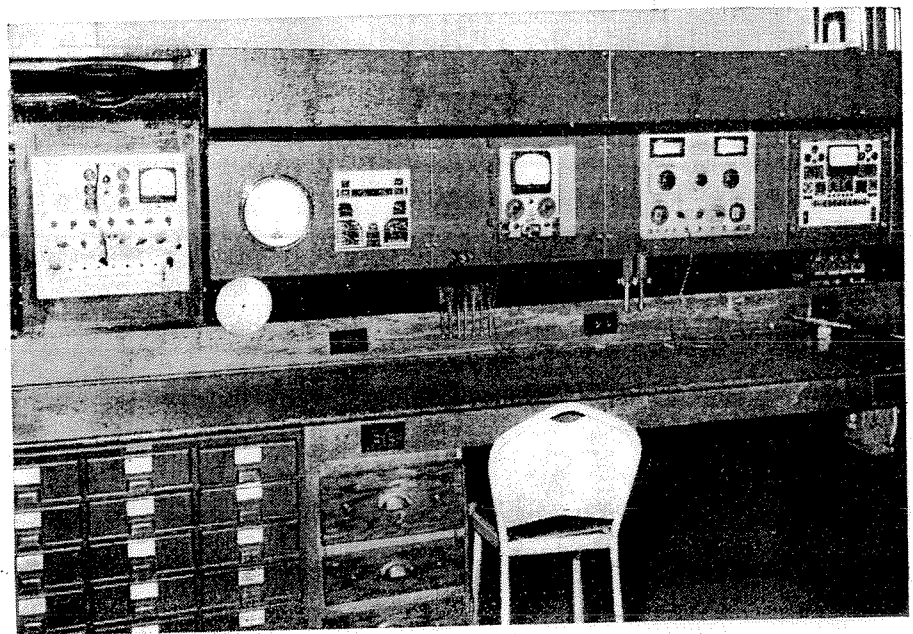



The following article describes the new and remarkably ingenious Solovox, invented by Laurens Hammond who created the Hammond Organ and the Novachord, and tells how this 14-tube device may be used as an electronic musical supplement to any piano.

← The photos at left illustrate various elements of the Solovox. At A, the attachment in use on a grand piano, a set of 12 control tablets giving any piano an indefinite variety of tone colors that simulate the organ (Note individual volume control.); B, close-up of upper portion of the Solovox showing how the control tablet add-on device is fitted to produce a desired effect; C, the Solovox keyboard being attached to the piano keyboard by thumbscrews.

THE ELECTRONIC "SOLOVOX" Latest Radio-Musical Adjunct to the Piano

THE Solovox is a new 14-tube instrument—invented by Laurens Hammond, creator of the Hammond Organ and the Novachord, and expressly designed as a musical supplement to the piano—that even a child can play perfectly. Operated entirely by electricity, the Solovox is a 3-octave keyboard which is attached to the piano so that the fingers of one hand can easily span the 2 keyboards. A total of 12 control tablets give the Solovox a 6-octave range as well as an indefinite variety of tone colors, and being smooth, sustained and capable of "swell," its tone colors make an effective contrast to the percussive brilliance of the piano. A knee lever controls the volume. A slim tone cabinet containing the electrical equipment, including the loudspeaker, is set alongside a vertical piano or underneath a grand piano.

This instrument represents a new source of income for Servicemen and Servicemen-dealers.

MODUS OPERANDI

All the notes of the Solovox are controlled by a single radio vacuum tube *master oscillator* (see diagram) operating at one of the 12 audio frequencies in the highest octave of the instrument (2,093 to 3,951 cycles). Each time a key is depressed, a switch under it tunes this oscillator to the pitch associated with the key in this highest-octave range. This occurs regardless of whereabouts on the keyboard the playing key is depressed. Thus, whenever any one of the "C" keys is depressed, this oscillator is tuned to 2,093 cycles, which is its lowest frequency. If any "B" key is depressed, its frequency will be 3,951 cycles, which is its highest frequency.

The output of this master oscillator controls the frequency of another oscillator called the *buffer oscillator* which operates at the same frequency as the master oscillator. The output of this first controlled (buffer) oscillator in turn controls the frequency of a second controlled oscillator, so interconnected with the first as to oscillate at one-half the frequency of the first oscil-

lator. This new frequency corresponds to a note of pitch one octave lower than the first controlled oscillator.

Similar cascaded oscillators provide pitches of 2, 3, 4 and 5 octaves below that of the master oscillator. In this way, each time the master oscillator is tuned to some one of its 12 possible frequencies (one for each note of the scale), each of these 6 controlled oscillators immediately follows it to produce outputs which are the lower octaves of this pitch, to form a series of 6 frequencies in exact octave relationships. Now the particular oscillator outputs desired for passing through the amplifier and speaker, depend upon the particular playing key depressed (for instance on which one of the 3 "C" keys) and also, upon which of the "BASS-TENOR-CONTRALTO-SOPRANO" controls are employed.

The selection of the desired oscillator occurs when a second contact under each key closes. This second contact operates an electrical relay having contacts to make the desired oscillator selection. It is to be noted that there are 3 relays, one of which is common to each of the 3 octave groups of keys. Thus, we see that a playing key functions in 2 ways—first, it tunes all of the oscillators to the pitch of the key being depressed, and then selects the output of the particular sub-octave frequency controlled oscillator desired.

A further function of the second key contact is to transmit the signal to the speakers with a controlled rate of attack, so as not to be musically abrupt. Tuned electrical circuits and tone controls follow, which control the quality of tone over a very wide range.

The effect of the "MUTE" is produced by passing the signal through a vacuum tube operated non-linearly so as to suppress the sharp curvature of its input wave, and thus render the tone more mellow.

PERMEABILITY TUNED

The "VIBRATO" effect is produced by a vibrating reed (which is put into motion when the volume control lever is brought forward in starting the instrument) which intermittently changes the pitch of the

master-oscillator by varying the inductance of a small coil (L1 in diagram) connected across it.

The volume of sound from the speaker is controlled by a knee-operated rheostat which acts to control the amount of amplification.

The Solovox will remain in tune indefinitely. However, as the pitch of the piano with which it is to be played will vary considerably, a tuning adjustment knob at the top of the tone cabinet has been provided with which the instrument may be easily tuned by the pianist in 10 seconds' time, to the piano. It is not necessary to tune each note—the single tuning knob provided simultaneously tunes them all by varying the inductance (L2 in diagram) that resonates the master-oscillator circuit.

USES


The Solovox, which can be played by even the self-made pianist without any special instruction, adds singing voices like orchestral instruments to the tones of the piano. The player carries the melody on the Solovox with the right hand and the left hand accompanies on the piano. The right hand can easily encompass notes on the Solovox and piano keyboards simultaneously, considerably enlarging the pianist's scope.

On the front of the Solovox are the previously-mentioned, tablet-shaped tone selectors and all that the player must do is to push them in various combinations to extend the range of the instrument to 6 octaves and create hundreds of exciting new tone-colors. Some of these tones resemble flutes, strings, brasses or woodwinds, while others have never been heard before!

The exceptional versatility of the Solovox makes it a flexible addition to the studio equipment of any radio station. With the Solovox attached to the piano, ensembles are heightened and dramatized by its smooth attack. The rich-variety of its tones ranging from a brilliant, string-like effect to a deep and penetratingly organ-like quality make it a new and different instrument for music lovers to hear and enjoy.

For a vocalist, the Solovox provides a

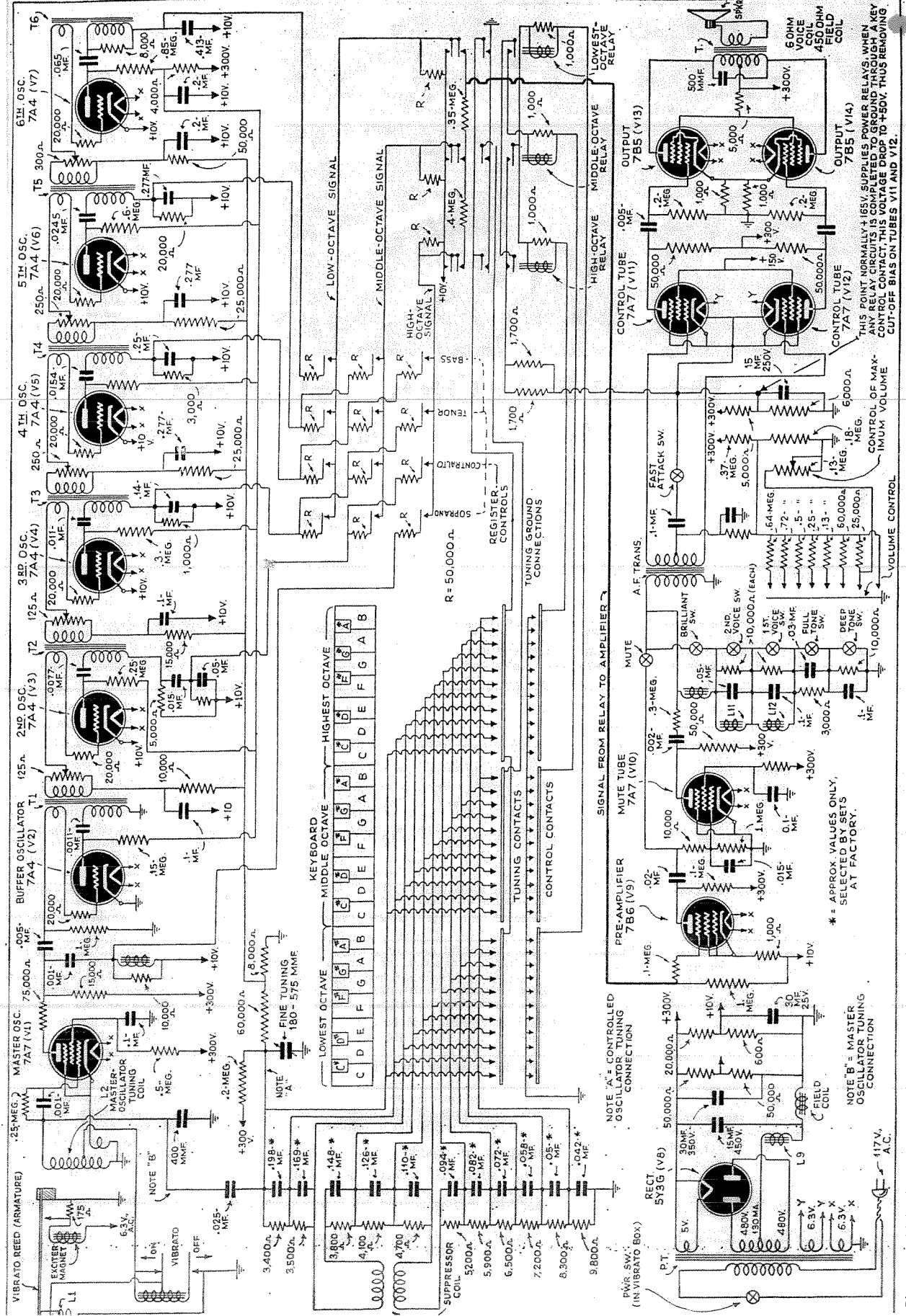*See "Announcing the Novachord—Electronic Music's New 163-Tube 'Baby'". Radio-Craft, April, 1939.



Diagram, model J Solovox. Following are circuit notations, including omissions, not located in time for inclusion in the diagram. Tube V9 (7B6): consider the grids, connected to the cathode, as diode plates. A movable iron core times L2. Missing component values: V3 plate R.F. load resistor, 4,000 ohms; V5 plate D.C. load resistor, 0.5-meg.; V10 S.-G. filter resistor, 0.5-meg.; connected to center-tap of V.A.F. trans., is a 0.72-meg. unit shunted by 6.15-mf.; V12-V14 coupling unit, 0.005-mf. Note that contacts shown normally open, nearest to Highest-, Middle-, and Lowest-Octave relay magnets, should be shown closed; ditto, the 3 pairs of contacts, at top, contacting the +10 V. bus.

* = APPROX VALUES ONLY, SELECTED BY SETS AT FACTORY.

NOTE 'A' = CONTROLLED OSCILLATOR TUNING CONNECTION

NOTE 'B' = MASTER OSCILLATOR TUNING CONNECTION

RADIO'S FINEST Electronic VOLT METER



\$39⁹⁵

Dealer Net Cash Price
S.I.C. Time Payment Plan
\$5.00 cash and 10 monthly
payments of \$3.90.

In Metal Case

MODEL **549**
ELECTRONIC VOLT METER

Model 549 is the result of a long period of research in designing a multimeter which will fulfill the serviceman's needs of today and tomorrow at a price he can afford to pay. The instrument will take care of all the serviceman's multimeter requirements since it has standard provisions for A.C. and output volts, direct current measurements, etc., in addition to the electronic circuit for D.C. voltage and resistance measurements.

0.1 TO 6000 D.C. VOLTS—covered by six overlapping ranges of 0/2/6/20/60/200/600 volts. These ranges may be extended to 6000 volts, at small extra cost, by use of a SUPREME Type 4875 Probe. The input impedance of all ranges up to and including the 600 volt range is 15,000,000 ohms. The input impedance of the 6000 volt range is 150,000,000 ohms. Both probes for measuring D.C. volts have a built-in resistance so that the D.C. volts developed across oscillator grid leak can be measured without materially affecting the oscillator. Also all plate, screen bias, A.V.C., and A.F.C. voltages can be measured without upsetting the operation of the receiver. Voltages of either negative or positive polarity with respect to chassis or ground may be measured by setting the circuit selector switch to "—" volts or "+" volts. The low range of 2 volt full scale gives a sensitive meter necessary in measuring small control voltages.

0.5 OHMS TO 1000 MEGOHMS—covered by 5 overlapping ranges of 0/1000/100,000/1 megohm/10 megohms/1000 megohms. This electronic circuit permits all resistance ranges, including the 1000 megohm range, to be operated by the self-contained 3 volt bat-

tery. Features incorporated are the extreme accuracy acquired by adjusting the ohmmeter at "zero" position and "full scale" position. After this is once set there are no adjustments to be made between ranges. The low range has a center scale resistance of fifteen (15) ohms which gives a good deflection in checking resistances of radio frequency coils. You will like this type of ohmmeter for its speed and accuracy. Being of an electronic type the meter is fully protected and accidental application of the voltage to the ohmmeter will not injure the instrument.

0.1 VOLT TO 500 A.C. VOLTS—covered by 5 overlapping ranges of 0/5/15/50/150/500 volts in a circuit whose calibration is guaranteed to $\pm 3\%$. Copper oxide rectifier is fully protected and carries the same guarantee as all other parts in the instrument. Temperature error of rectifier is corrected over a working range of 40° F to 100° F.

10 MICROAMPERES TO 15 AMPERES D.C. CURRENT—covered by 7 direct ranges of 0/500 microamperes; 0/5/15/50/150/500 M.A.; and 0/15 amperes. Such a wide selection of ranges was incorporated to meet all current measurements necessary—from the few microamperes found in control circuits to the ampere drain of automobile receivers.

0.1 TO 500 OUTPUT VOLTS—can be used with any good signal generator (SUPREME Model 571 or 561) for receiver alignment. Covered by five ranges of 0/5/15/50/150/500 Volts.

The Model 549 is also available in beautiful oak case as illustrated for \$42.50 cash or \$5.00 cash and 10 monthly payments of \$4.18.

SUPREME

SUPREME INSTRUMENTS CORP.
GREENWOOD, MISSISSIPPI, U.S.A.

SEND FOR NEW CATALOG

—just off the press. Large, two color illustrations, complete descriptions of 22 new 1941 model SUPREME quality testing instruments. Write today!

PATENTS—TRADE MARKS

Booklet concerning Inventions & Patents
Form "Evidence of Conception" with
instructions for use and "Schedule of
Government and Attorneys Fees"—Free

LANCASTER, ALLWINE & ROMMEL
Registered Patent Attorneys
436 Bowen Bldg. Washington, D. C.

SCOTT CUSTOM BUILT RADIOS

SERVICING TELECEIVERS

SERVICE work on television receivers can be divided into 2 parts: 95% can be done with the conventional instruments which every Serviceman has already, plus an ultra-frequency oscillation; 5% requires instruments that individual Servicemen and most dealers would not be justified in buying, Andrea Radio Corp. has found.

It appears, therefore, that the jobbers will have to take upon themselves the investment in instruments required for the 5% part of service problems. Dealers and Servicemen will handle all this very small part of the work, and when a condition arises which they cannot meet, they will have to deliver the set to the jobber's service shop, since the equipment needed in such cases is hardly portable, nor would it be

ELECTRONIC SOLOVOX

(Continued from page 290)

full, well-rounded background. The fact that all the technical difficulties, such as perfect pitch intonation, smooth vibrato, smooth tonal attack, and quality control are all taken care of in the design of the instrument makes the Solovox the easiest of all orchestral instruments to play. No special training is necessary, for anyone who can pick out a tune by ear on the piano can play it effectively.

In the studio where space is precious, the Solovox is especially adaptable, for it takes up no extra room. It is entirely electrical in operation and by means of 1 tuning knob can be tuned to the piano with which it has been assembled. The 14 standard, inexpensive radio tubes—the heart of the instrument—may need replacement only in the course of several years' playing time. Radio men will note that the comparatively low cost of the Solovox (under \$200) places it within the range of small as well as large radio stations. (Dealers give to purchasers, without charge, what little instruction may be necessary.)



Laurens Hammond at work on his newest invention, the 14-tube Solovox, which was recently introduced simultaneously in Chicago to the National Music Merchants Association convention and in New York to music notables and to members of the press.

wise to do the work in the customer's home.

95% Are Simple Cases—As you will discover when you become acquainted with television receivers, they are quite different, electrically and mechanically, from broadcast sets. Since the slightest deviation from extremely high standards of precision design shows up in the "picture" tube, such compromises in specifications and tolerances as have been adopted widely in sound receivers cannot be made in television circuits.

The use of high voltage exerts an important influence in television set design. If parts break down in sound equipment, it is easy to replace whatever has gone wrong, but when several thousand volts get loose, expensive damage may result. Finally, cheap materials and inferior designs are not suitable for ultra-frequency circuits.

Thus, the superior materials and construction necessary for television equipment eliminate the source of many failures common to the average sound receiver. There is a sufficient background of experience already to indicate that service work on an average good television receiver is almost entirely a matter of tube failures.

From the foregoing, you can see that there is no high-voltage hazard involved in 95% of the television service work. The 5% to be done by the jobber's service department may require special tests to be made with the current on, but the Serviceman who makes the conventional tests for which he is equipped does not need to take any risk whatever. He can do his work with the power switched off.